



## **Phase 2 EDA**

**Name: Mohand Mahmoud Farag**

**ID: 16p6042**

**Group: 1**

**Section: 2**

# Introduction:

In this phase we use fedora in Vm to implement different circuits to obtain the best in delay and area to be more useful. At first we change the original code to unix then make three files (makefile , paramfile, path.path) (in this zip file).

We use this makefile to generate some operation and then order them by some commands.

## Commands:

Make vhd\_to\_fsm

Make syf

Make boom

Make boog

Make loon

Make flatbeh

Make dft

Then we use the output code from loon and dft in test bench to insure that code is right.

The Syf output


| Type | delay | area  | Multiplication |
|------|-------|-------|----------------|
| A    | 3221  | 65500 | 210975500      |
| J    | 2687  | 64000 | 171968000      |
| M    | 2305  | 61250 | 141181250      |
| O    | 2458  | 93500 | 229823000      |
| R    | 2271  | 61750 | 140234250      |

**I choose the R type because it is the minimum multiplication**

## The test bench of loon:

| Test number                        | Daytime | Code | Reset | Expected Door & Doors | Expected Alarm & Alarms | Door & Doors | Alarm & Alarms |
|------------------------------------|---------|------|-------|-----------------------|-------------------------|--------------|----------------|
| Reset test                         | X       | X    | 1     | 0                     | 0                       | 0            | 0              |
| O with dt=1 (test case 1)          | 1       | 1101 | 0     | 1                     | 0                       | 1            | 0              |
| Full input with dt=1 (test case 2) | 1       | 0010 | 0     | 0                     | 0                       | 0            | 0              |
|                                    | 1       | 0110 | 0     | 0                     | 0                       | 0            | 0              |
|                                    | 1       | 1010 | 0     | 0                     | 0                       | 0            | 0              |
|                                    | 1       | 0000 | 0     | 0                     | 0                       | 0            | 0              |
|                                    | 1       | 0101 | 0     | 1                     | 0                       | 1            | 0              |
| O with dt=1 (test case 3)          | 0       | 1101 | 0     | 0                     | 1                       | 0            | 1              |
| Full input with dt=0 (test case 4) | 0       | 0010 | 0     | 0                     | 0                       | 0            | 0              |
|                                    | 0       | 0110 | 0     | 0                     | 0                       | 0            | 0              |
|                                    | 0       | 1010 | 0     | 0                     | 0                       | 0            | 0              |
|                                    | 0       | 0000 | 0     | 0                     | 0                       | 0            | 0              |
|                                    | 0       | 0101 | 0     | 1                     | 0                       | 1            | 0              |
| Incorrect input (test case 5)      | 0       | 0010 | 0     | 0                     | 0                       | 0            | 0              |
|                                    | 0       | 0110 | 0     | 0                     | 0                       | 0            | 0              |
|                                    | 0       | 1010 | 0     | 0                     | 1                       | 0            | 1              |

# The circuit:

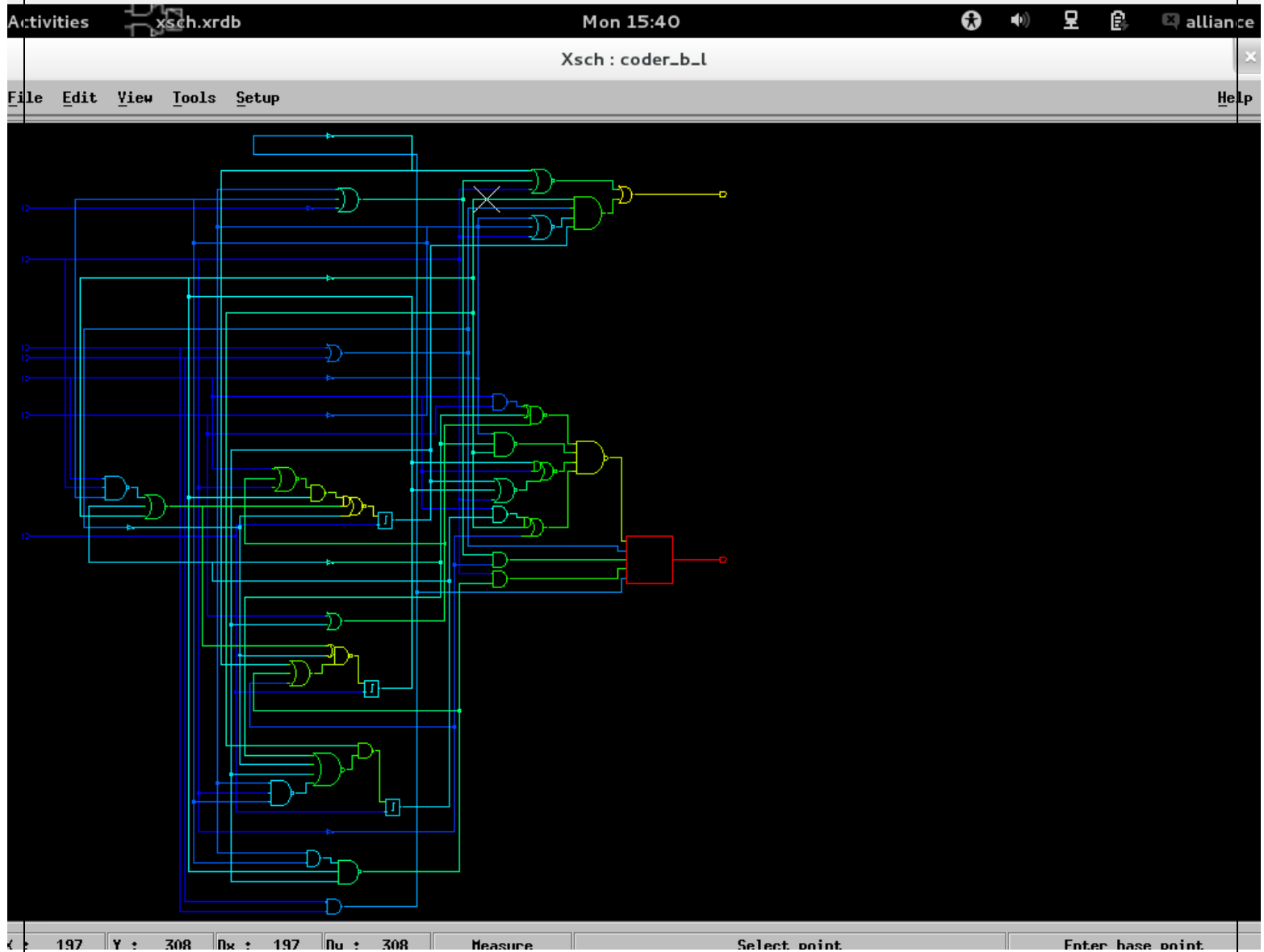

# The code:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

use ieee.NUMERIC_STD.all;

ENTITY projecttbb IS

END ENTITY projecttbb;

ARCHITECTURE fsmtbb OF projecttbb IS

component project1 is

port (

    clk    : in    bit;

           code   : in    bit_vector(3 downto 0) ;

    daytime : in    bit;

    reset   : inbit;

    vdd     : in bit;

    vss     : in bit;

    door    : out   bit;

    alarm   : out   bit

);

end component;

component coder_b_l is

port (

    clk    : in    bit;

    code   : in    bit_vector(3 downto 0);

    daytime : in    bit;

    reset   : in    bit;

    vdd     : in    bit;
```

```
    vss : in bit;

    door : out bit;

    alarm : out bit

);

end component;
```

```
FOR dut: project1 USE ENTITY WORK.project1 (FSM);

FOR duts: coder_b_l USE ENTITY WORK.coder_b_l (structural);

SIGNAL clk : bit := '0';

SIGNAL code : bit_vector(3 downto 0) := "0000";

SIGNAL daytime : bit := '1';

SIGNAL reset : bit := '1';

SIGNAL vdd : bit := '1';

SIGNAL vss : bit := '0';

signal door : bit:= '0';

signal alarm : bit := '0';

--SIGNAL clk : bit := '0';

SIGNAL codes : bit_vector(3 downto 0) := "0000";

SIGNAL daytimes : bit := '1';

SIGNAL resets : bit := '1';

--SIGNAL vdds : bit := '1';

--SIGNAL vsss : bit := '0';

signal doors : bit:= '0';

signal alarms : bit := '0';

begin

dut: project1 PORT MAP (clk, code, daytime, reset,vdd, vss, door, alarm);

duts: coder_b_l PORT MAP (clk, codes, daytimes, resets,vdd, vss, doors, alarms);
```

```
clk_process :process
```

```
begin
```

```
    clk <= '1';
```

```
    wait for 10 ns;
```

```
    clk <= '0';
```

```
    wait for 10 ns;
```

```
end process;
```

```
p1:process is begin
```

```
wait For 20 ns;
```

```
ASSERT door = doors and alarm = alarms
```

```
REPORT "1 error"
```

```
SEVERITY error;
```

```
---- first testbench
```

```
daytime<='1';
```

```
code<="1101";
```

```
reset<='0';
```

```
daytimes<='1';
```

```
codes<="1101";
```

```
resets<='0';
```

```
wait For 20 ns;
```

```
ASSERT door = doors and alarm = alarms
```

```
REPORT "2 error"
```

```
SEVERITY error;
```

```
-----second testbench
```

```
daytime<='1';
```

```
code<="0010";
```

```
reset<='0';
```

```
daytimes<='1';
```



```
codes<="0010";  
resets<='0';  
wait For 20 ns;  
ASSERT door = doors and alarm = alarms  
REPORT " 3 error"  
SEVERITY error;
```

```
-----  
daytime<='1';  
code<="0110";  
reset<='0';  
daytimes<='1';  
codes<="0110";  
resets<='0';  
wait For 20 ns;  
ASSERT door = doors and alarm = alarms  
REPORT " 4 error"  
SEVERITY error;
```

```
-----  
daytime<='1';  
code<="1010";  
reset<='0';  
daytimes<='1';  
codes<="1010";  
resets<='0';  
wait For 20 ns;  
ASSERT door = doors and alarm = alarms  
REPORT " 5 error"  
SEVERITY error;
```

```
daytime<='1';
code<="0000";
reset<='0';
daytimes<='1';
codes<="0000";
resets<='0';
wait For 20 ns;
ASSERT door = doors and alarm = alarms
REPORT " 6 error"
SEVERITY error;
```

-----

```
daytime<='1';
code<="0101";
reset<='0';
daytimes<='1';
codes<="0101";
resets<='0';
wait For 20 ns;
ASSERT door = doors and alarm = alarms
REPORT " 7 error"
SEVERITY error;
```

-----third testbench

```
daytime<='0';
code<="1101";
reset<='0';
daytimes<='0';
codes<="1101";
resets<='0';
wait For 20 ns;
```

**ASSERT door = doors and alarm = alarms**

**REPORT "8 error"**

**SEVERITY error;**

-----fourth testnech

**daytime<='0';**

**code<="0010";**

**reset<='0';**

**daytimes<='0';**

**codes<="0010";**

**resets<='0';**

**wait For 20 ns;**

**ASSERT door = doors and alarm = alarms**

**REPORT "9 error"**

**SEVERITY error;**

-----  
**daytime<='0';**

**code<="0110";**

**reset<='0';**

**daytimes<='0';**

**codes<="0110";**

**resets<='0';**

**wait For 20 ns;**

**ASSERT door = doors and alarm = alarms**

**REPORT "10 error"**

**SEVERITY error;**

-----  
**daytime<='0';**

**code<="1010";**

**reset<='0';**

```
daytimes<='0';  
codes<="1010";  
resets<='0';  
wait For 20 ns;  
ASSERT door = doors and alarm = alarms  
REPORT "11 error"  
SEVERITY error;
```

```
-----  
daytime<='0';  
code<="0000";  
reset<='0';  
daytimes<='0';  
codes<="0000";  
resets<='0';  
wait For 20 ns;  
ASSERT door = doors and alarm = alarms  
REPORT "12 error"  
SEVERITY error;
```

```
-----  
daytime<='0';  
code<="0101";  
reset<='0';  
daytimes<='0';  
codes<="0101";  
resets<='0';  
wait For 20 ns;  
ASSERT door = doors and alarm = alarms  
REPORT "13 error"  
SEVERITY error;
```

-----fifth testbench

daytime<='0';

code<="0010";

reset<='0';

daytimes<='0';

codes<="0010";

resets<='0';

wait For 20 ns;

ASSERT door = doors and alarm = alarms

REPORT "14 error"

SEVERITY error;

-----  
daytime<='0';

code<="0110";

reset<='0';

daytimes<='0';

codes<="0110";

resets<='0';

wait For 20 ns;

ASSERT door = doors and alarm = alarms

REPORT "15 error"

SEVERITY error;

-----  
daytime<='0';

code<="0110";

reset<='0';

daytimes<='0';

codes<="0110";

resets<='0';

**wait For 20 ns;**

**ASSERT door = doors and alarm = alarms**

**REPORT "16 error"**

**SEVERITY error;**



-----

**WAIT;**

**END PROCESS ;**

**END ARCHITECTURE ;**

# The output:

  


## The test bench of DFT:

| Test number                        | Daytime | Code | Reset | Expected Door & Doors & Doord | Expected Alarm & Alarms & Alarmd | Door & Doors & Doord | Alarm & Alarms & Alarmd |
|------------------------------------|---------|------|-------|-------------------------------|----------------------------------|----------------------|-------------------------|
| Reset test                         | X       | X    | 1     | 0                             | 0                                | 0                    | 0                       |
| O with dt=1 (test case 1)          | 1       | 1101 | 0     | 1                             | 0                                | 1                    | 0                       |
| Full input with dt=1 (test case 2) | 1       | 0010 | 0     | 0                             | 0                                | 0                    | 0                       |
|                                    | 1       | 0110 | 0     | 0                             | 0                                | 0                    | 0                       |
|                                    | 1       | 1010 | 0     | 0                             | 0                                | 0                    | 0                       |
|                                    | 1       | 0000 | 0     | 0                             | 0                                | 0                    | 0                       |
|                                    | 1       | 0101 | 0     | 1                             | 0                                | 1                    | 0                       |
| O with dt=1 (test case 3)          | 0       | 1101 | 0     | 0                             | 1                                | 0                    | 1                       |
| Full input with dt=0 (test case 4) | 0       | 0010 | 0     | 0                             | 0                                | 0                    | 0                       |
|                                    | 0       | 0110 | 0     | 0                             | 0                                | 0                    | 0                       |
|                                    | 0       | 1010 | 0     | 0                             | 0                                | 0                    | 0                       |
|                                    | 0       | 0000 | 0     | 0                             | 0                                | 0                    | 0                       |
|                                    | 0       | 0101 | 0     | 1                             | 0                                | 1                    | 0                       |
| Incorrect input (test case 5)      | 0       | 0010 | 0     | 0                             | 0                                | 0                    | 0                       |
|                                    | 0       | 0110 | 0     | 0                             | 0                                | 0                    | 0                       |
|                                    | 0       | 1010 | 0     | 0                             | 1                                | 0                    | 1                       |



# The circuit:

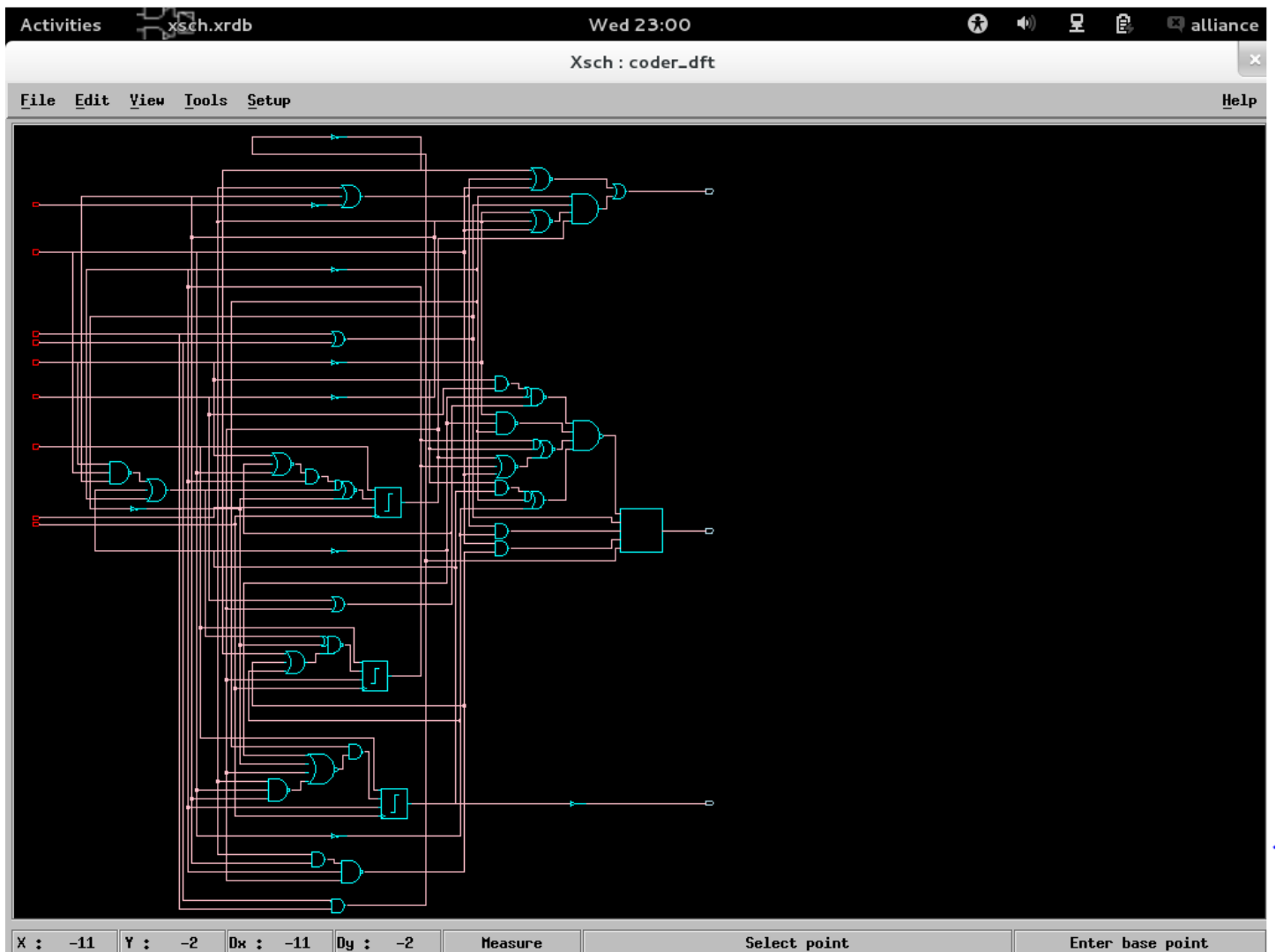

# The Code:

```
library Sxlib_ModelSim;

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

use ieee.NUMERIC_STD.all;

ENTITY projecttbb IS

END ENTITY projecttbb;

ARCHITECTURE fsmtbb OF projecttbb IS

component project1 is

port (

    clk    : in    bit;

        code : in    bit_vector(3 downto 0) ;

        daytime : in  bit;

        reset : in    bit;

        vdd : in    bit;

        vss : in bit;

        door : out    bit;

        alarm : out    bit

    );

end component;

component coder_b_l is

port (

    clk : in  bit;

    code : in  bit_vector(3 downto 0);

    daytime : in  bit;

    reset : in  bit;

    vdd : in  bit;
```

```

    vss : in bit;

    door : out bit;

    alarm : out bit
);
end component;
component coder_dft is
    port (
        clk : in bit;
        code : in bit_vector(3 downto 0);
        daytime : in bit;
        reset : in bit;
        vdd : in bit;
        vss : in bit;
        door : out bit;
        alarm : out bit;
        scanin : in bit;
        test : in bit;
        scanout : out bit
    );
end component;
FOR dut: project1 USE ENTITY WORK.project1 (FSM);
FOR duts: coder_b_l USE ENTITY WORK.coder_b_l (structural);
FOR dutd: coder_dft USE ENTITY WORK.coder_dft (structural11);
SIGNAL clk : bit := '0';
SIGNAL code : bit_vector(3 downto 0) := "0000";
SIGNAL daytime : bit := '1';
SIGNAL reset : bit := '1';
SIGNAL vdd : bit := '1';
SIGNAL vss : bit := '0';

```

```

signal door : bit:= '0';
signal alarm : bit := '0';
--SIGNAL clk   : bit := '0';
SIGNAL codes   : bit_vector(3 downto 0) := "0000";
SIGNAL daytimes : bit := '1';
SIGNAL resets : bit := '1';
--SIGNAL vdds   : bit := '1';
--SIGNAL vsss   : bit := '0';
signal doors : bit:= '0';
signal alarms : bit := '0';
SIGNAL coded   : bit_vector(3 downto 0) := "0000";
SIGNAL daytimed : bit := '1';
SIGNAL resetd : bit := '1';
signal doord : bit:= '0';
signal alarmd : bit := '0';
SIGNAL scanin: bit := '0';
SIGNAL test: bit := '0' ;
SIGNAL scanout: bit := '0' ;
SIGNAL seqance: bit_vector (3 downto 0) := "1101" ;
begin
dut: project1 PORT MAP (clk, code, daytime, reset,vdd, vss, door, alarm);
duts: coder_b_l PORT MAP (clk, codes, daytimes, resets,vdd, vss, doors, alarms);
dutd: coder_dft PORT MAP (clk, coded, daytimed, resetd,vdd, vss, doord, alarmd,scanin,test,scanout);
clk_process :process
begin
    clk <= '1';
    wait for 10 ns;
    clk <= '0';
    wait for 10 ns;

```

```

    end process;

p1:process is begin
wait For 20 ns;

ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd

REPORT "1 error"

SEVERITY error;

---- first testbensh

daytime<='1';
code<="1101";
reset<='0';
daytimes<='1';
codes<="1101";
resets<='0';
daytimed<='1';
coded<="1101";
resetd<='0';
wait For 20 ns;

ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd

REPORT "2 error"

SEVERITY error;

-----second testbench

daytime<='1';
code<="0010";
reset<='0';
daytimes<='1';
codes<="0010";
resets<='0';
daytimed<='1';

```

```
coded<="0010";
resetd<='0';
wait For 20 ns;
ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd
REPORT " 3 error"
SEVERITY error;
```

-----

```
daytime<='1';
code<="0110";
reset<='0';
daytimes<='1';
codes<="0110";
resets<='0';
daytimed<='1';
coded<="0110";
resetd<='0';
wait For 20 ns;
ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd
REPORT " 4 error"
SEVERITY error;
```

-----

```
daytime<='1';
code<="1010";
reset<='0';
daytimes<='1';
codes<="1010";
resets<='0';
daytimed<='1';
coded<="1010";
```

```
resetd<='0';  
wait For 20 ns;  
ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd  
REPORT " 5 error"  
SEVERITY error;
```

-----

```
daytime<='1';  
code<="0000";  
reset<='0';  
daytimes<='1';  
codes<="0000";  
resets<='0';  
daytimed<='1';  
coded<="0000";  
resetd<='0';  
wait For 20 ns;  
ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd  
REPORT " 6 error"  
SEVERITY error;
```

-----

```
daytime<='1';  
code<="0101";  
reset<='0';  
daytimes<='1';  
codes<="0101";  
resets<='0';  
daytimed<='1';  
coded<="0101";  
resetd<='0';
```

```
wait For 20 ns;

ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd

REPORT " 7 error"

SEVERITY error;

-----third testbench

daytime<='0';
code<="1101";
reset<='0';
daytimes<='0';
codes<="1101";
resets<='0';
daytimed<='0';
coded<="1101";
resetd<='0';
wait For 20 ns;

ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd

REPORT "8 error"

SEVERITY error;

-----fourth testnech

daytime<='0';
code<="0010";
reset<='0';
daytimes<='0';
codes<="0010";
resets<='0';
daytimed<='0';
coded<="0010";
resetd<='0';
wait For 20 ns;
```



ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd

REPORT "9 error"

SEVERITY error;

-----

daytime<='0';

code<="0110";

reset<='0';

daytimes<='0';

codes<="0110";

resets<='0';

daytimed<='0';

coded<="0110";

resetd<='0';

wait For 20 ns;

ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd

REPORT "10 error"

SEVERITY error;

-----

daytime<='0';

code<="1010";

reset<='0';

daytimes<='0';

codes<="1010";

resets<='0';

daytimed<='0';

coded<="1010";

resetd<='0';

wait For 20 ns;

ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd

REPORT "11 error"

SEVERITY error;

-----

daytime<='0';

code<="0000";

reset<='0';

daytimes<='0';

codes<="0000";

resets<='0';

daytimed<='0';

coded<="0000";

resetd<='0';

wait For 20 ns;

ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd

REPORT "12 error"

SEVERITY error;

-----

daytime<='0';

code<="0101";

reset<='0';

daytimes<='0';

codes<="0101";

resets<='0';

daytimed<='0';

coded<="0101";

resetd<='0';

wait For 20 ns;

ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd

REPORT "13 error"

SEVERITY error;

-----fifth testbench

daytime<='0';

code<="0010";

reset<='0';

daytimes<='0';

codes<="0010";

resets<='0';

daytimed<='0';

coded<="0010";

resetd<='0';

wait For 20 ns;

ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd

REPORT "14 error"

SEVERITY error;

-----  
daytime<='0';

code<="0110";

reset<='0';

daytimes<='0';

codes<="0110";

resets<='0';

daytimed<='0';

coded<="0110";

resetd<='0';

wait For 20 ns;

ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd

REPORT "15 error"

SEVERITY error;

-----  
daytime<='0';

code<="0110";

reset<='0';

daytimes<='0';

codes<="0110";

resets<='0';

daytimed<='0';

coded<="0110";

resetd<='0';

wait For 20 ns;

ASSERT door = doors and door = doord and alarm =alarms and alarm = alarmd

REPORT "16 error"

SEVERITY error;



-----

WAIT;

END PROCESS ;

END ARCHITECTURE ;

## The output:

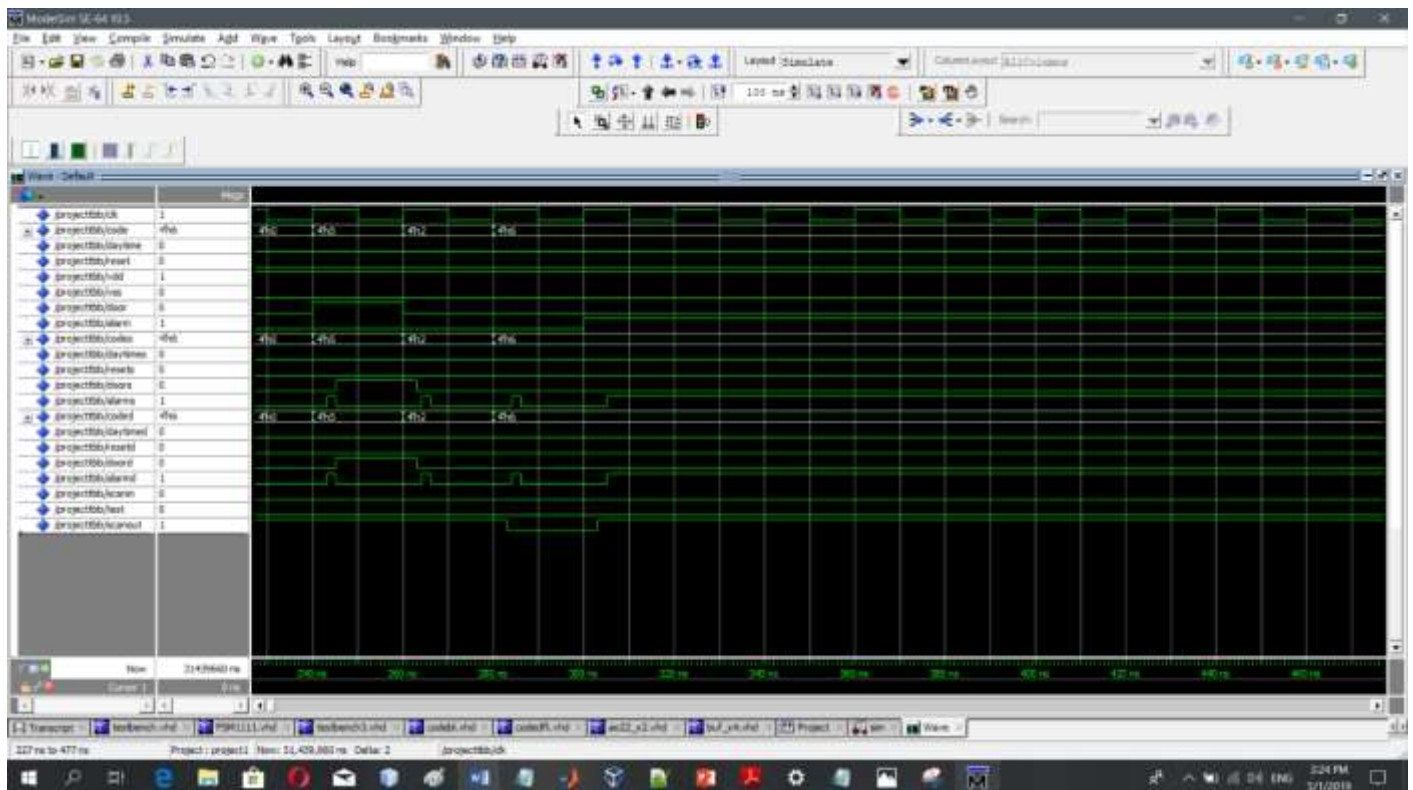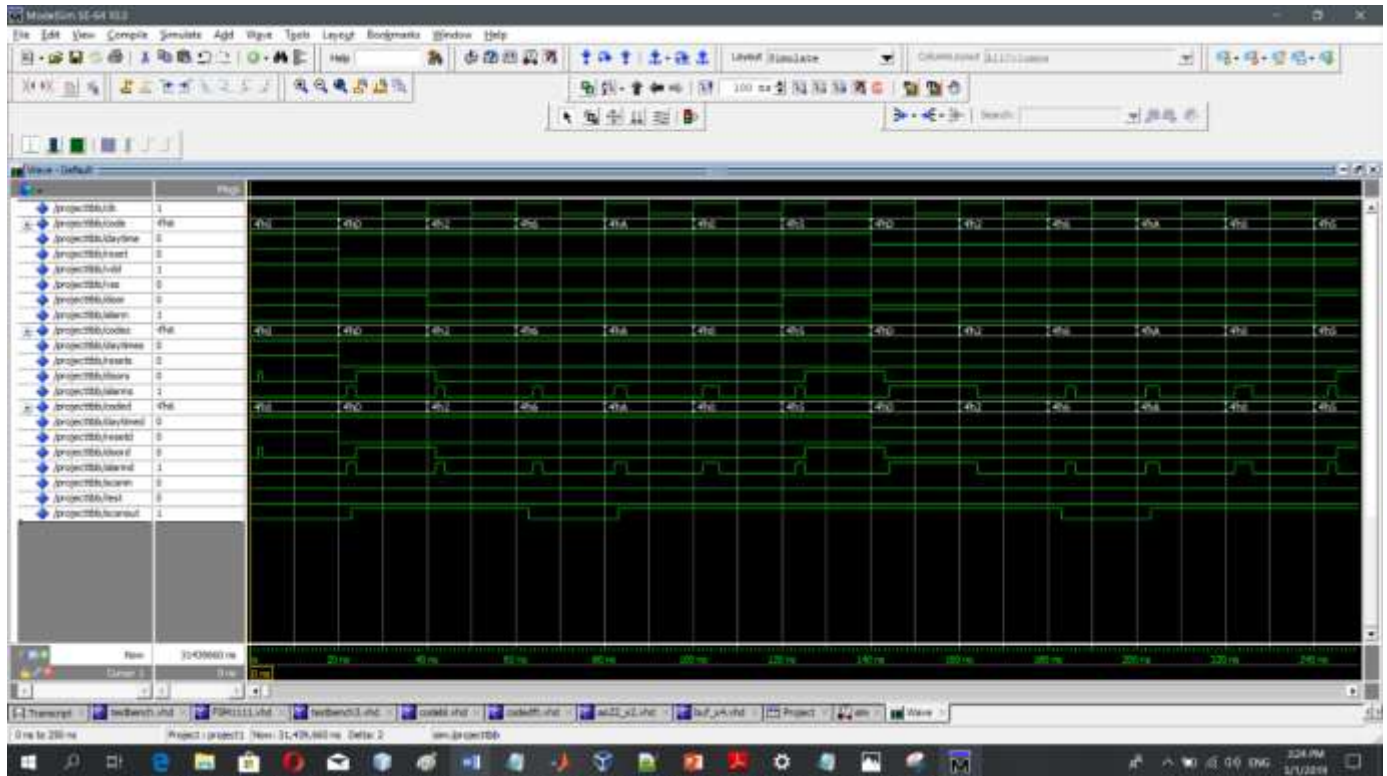

## The Test bench of scan:

| test | scanin | Expected scanout | scanout |
|------|--------|------------------|---------|
| 1    | 1010   | 1010             | 1010    |

## The Code:

```
library Sxlib_ModelSim;

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use ieee.NUMERIC_STD.all;

ENTITY testbenchsc IS
END ENTITY testbenchsc;

ARCHITECTURE fsmtbsc OF testbenchsc IS
component coder_dft is
port (
    clk    : in    bit;
    code   : in    bit_vector(3 downto 0);
    daytime : in    bit;
    reset  : in    bit;
    vdd    : in    bit;
    vss    : in    bit;
    door   : out   bit;
    alarm  : out   bit;
    scanin : in    bit;
    test   : in    bit;
    scanout : out   bit
```

```

);
end component;
FOR dut: coder_dft USE ENTITY WORK.coder_dft (structural11);
SIGNAL clk : bit := '0';
SIGNAL vdd : bit := '1';
SIGNAL vss : bit := '0';
SIGNAL coded : bit_vector(3 downto 0) := "0000";
SIGNAL daytimed : bit := '1';
SIGNAL resetd : bit := '1';
signal doord : bit:= '0';
signal alarmd : bit ;
SIGNAL scanin: bit ;
SIGNAL test: bit ;
SIGNAL scanout: bit;
SIGNAL seqance: bit_vector (3 downto 0) := "1010" ;
begin
dut: coder_dft PORT MAP (clk, coded, daytimed, resetd,vdd, vss, doord, alarmd,scanin,test,scanout);
clk_process :process
begin
    clk <= '1';
    wait for 10 ns;
    clk <= '0';
    wait for 10 ns;

    end process;
p1:process is begin
test <= '1';
    for i In 0 to seqance'length-1
        loop scanin <= seqance(i);

```

wait for 20 ns;

if i>3 then

Assert scanout=seance(i-3)

Report "scanout does not follow scan in"

Severity error;

end if;

end loop;

WAIT;

END PROCESS ;

END ARCHITECTURE ;

## The output:

